# **Simple Circuits**

# COMP 273 Assignment 4 – Fall 2021

Due: October 28, 2021, at 4 PM on myCourses

### **Submission instructions**

All work must be your own and must be submitted to myCourses. <u>Include your name and student number in a comment at the top of your documents / Logisim circuits</u>. **Submit only one file: a4.circ**. Do not use a zip archive. Check your submission by downloading it from myCourses and checking that it was correctly submitted. You will not receive marks for work that is incorrectly submitted.

### **Purpose**

- An easy first circuit assignment
- To get used to using Logisim Evolution (this will be our new run-time environment)
- To build your first running sircuit (the Awillianut and Indian and then stell be correct result)

## Helpful

• Tutorial D shou https://eduassistpro.github.io/

Using Logisim Evolution cheat the count for the followin edu\_assist\_pro

- Input: a 3-bit unsigned integer number
- Output: a single bit
- Task: The output bit becomes 1 when the input number is odd and greater than three

### **Steps**

- Do not use bit circuits (flip-flops), instead use input and output pins and logic gates.
- Place 3 input pins on the left side of your circuit. These will represent the 3-bit unsigned integer number. The TA will click these pins to select a binary number.
- Connect your circuit to a <u>clock</u>. The TA will turn the clock on to <u>run</u> the circuit, to see the result in the output pin. The output pin must display 0 when the clock is off.
- Place the output pin on the right side of the circuit.

### **Important**

There are two possible solutions for this problem. One solution uses only 2 input pins, the other solution uses all 3 input pins. Create both solution circuits in the same Logisim Evolution file.
 Place the 2-pin solution above the 3-pin solution.

# Marking

- Maximum 20 points
  - o 10 points for 2-bit solution
  - o 10 points for 3-bit solution
- -10% per day late with max 2 late days
- -3 points for not following instructions
- -5 points for not using the clock
- Assignment must execute to be graded

# Assignment Project Exam Help https://eduassistpro.github.io/ Add WeChat edu\_assist\_pro